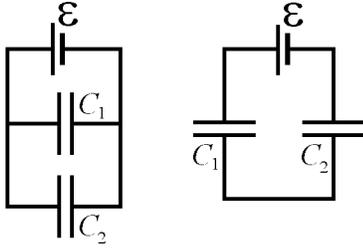


Base your answers to questions 1 through 3 on the diagram below which shows two different capacitors,  $C_1$  and  $C_2$ , in two different connections to the same source of emf  $\mathcal{E}$  that has no internal resistance.

For each question pick your answer from the following list.

- I. It is greater for the parallel connection.
- II. It is greater for the series connection.
- III. It is the same for both connections.
- IV. It is different for each connection, but one must know the values of  $C_1$  and  $C_2$ , to know which is greater.
- V. It is different for each connection, but one must know the value of  $\mathcal{E}$  to know which is greater.



1. How does the equivalent capacitance for these two cases compare?

- A) I
- B) II
- C) III
- D) IV
- E) V


2. How does the total charge stored on the capacitors for these two cases compare?

- A) I
- B) II
- C) III
- D) IV
- E) V

3. How does the voltage drop over  $C_1$  for these two cases compare?

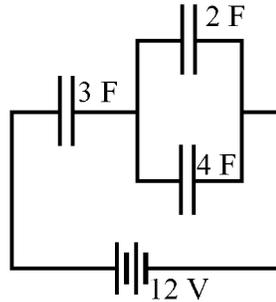- A) I
- B) II
- C) III
- D) IV
- E) V

Base your answers to questions 4 through 6 on the circuit diagram below which shows three capacitors connected to a 12 volt battery.



4. What is the equivalent capacitance of this arrangement.

- A) 2 F
- B) 3 F
- C)  $\frac{10}{3}$  F
- D)  $\frac{13}{3}$  F
- E) 9 F

5. What is the total energy stored in the circuit?

- A) 24 J
- B) 52 J
- C) 144 J
- D) 288 J
- E) 312 J





6. What is the charged stored on the 4 F capacitor?

- A) 8 C
- B) 16 C
- C) 24 C
- D) 32 C
- E) 48 C

8. What is the equivalent capacitance of circuit IV?

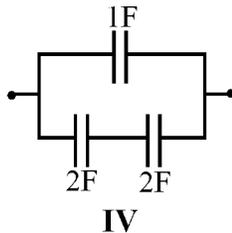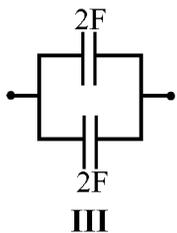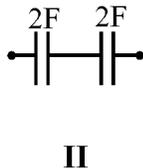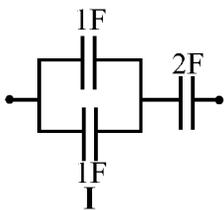- A) 1 F
- B) 2 F
- C) 2.5 F
- D) 3 F
- E) 4 F

Base your answers to questions 7 and 8 on the four arrangements of capacitors shown below.




7. Which two arrangements of capacitors shown above have the same capacitance between the terminals?

- A) I and II
- B) I and III
- C) I and IV
- D) II and III
- E) III and IV

9. A portion of a circuit is built using three identical capacitors of capacitance  $C$ . What is a possible equivalent capacitance for this portion of the circuit?

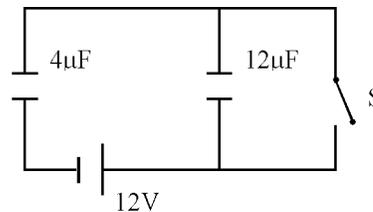- A)  $\frac{C}{2}$
- B)  $C$
- C)  $\frac{3}{2}C$
- D)  $2C$
- E)  $\frac{5}{2}C$

Base your answers to questions 10 and 11 on the following circuit diagram in which the battery has zero internal resistance.




10. When the switch  $S$  is closed, what is the charge on the  $4 \mu\text{F}$  capacitor?

- A)  $3 \mu\text{C}$
- B)  $4 \mu\text{C}$
- C)  $12 \mu\text{C}$
- D)  $36 \mu\text{C}$
- E)  $48 \mu\text{C}$

11. When the switch  $S$  is open, what is the voltage across the  $12\ \mu\text{F}$  capacitor?

- A) 1 V
- B) 3 V
- C) 4 V
- D) 9 V
- E) 12 V

12.

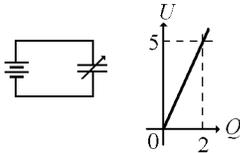

The circuit shown above left is made up of a variable capacitor and a battery of negligible internal resistance. A graph of the energy  $U$  (in Joules) stored in the capacitor as a function of the charge  $Q$  (in Coulombs) stored on it is given above. The emf of the battery is most nearly

- A) 1.6 V
- B) 2.2 V
- C) 2.5 V
- D) 5 V
- E) 6.3 V

13. Which of the following is necessarily true for capacitors connected in series in a circuit?

- A) They all must have the same capacitance.
- B) They all must hold an equal amount of charge.
- C) The total capacitance is the sum of the individual capacitances.
- D) They all must store the same amount of energy.
- E) The potential drop across each of them must be equal.

14. Compared to a two identical capacitors in parallel, two identical capacitors in series at the same voltage

- A) carry the same charge per plate
- B) hold more energy
- C) carry more charge per plate
- D) carry less charge per plate
- E) hold the same amount of energy

**Answer Key**  
**Ohm's Law MC Questions [Mar 28, 2011]**

1.   A  

2.   A  

3.   A  

4.   A  

5.   C  

6.   B  

7.   A  

8.   B  

9.   C  

10.  E  

11.   B  

12.   D  

13.   B  

14.   D  

---

Name \_\_\_\_\_

Class \_\_\_\_\_

Date \_\_\_\_\_

1. \_\_\_\_\_

2. \_\_\_\_\_

3. \_\_\_\_\_

4. \_\_\_\_\_

5. \_\_\_\_\_

6. \_\_\_\_\_

7. \_\_\_\_\_

8. \_\_\_\_\_

9. \_\_\_\_\_

10. \_\_\_\_\_

11. \_\_\_\_\_

12. \_\_\_\_\_

13. \_\_\_\_\_

14. \_\_\_\_\_