

1. An inductor
 - A) is a circuit element that stores electric potential energy
 - B) is a circuit element that provides a potential difference
 - C) is a circuit element that opposes changes in current
 - D) is a circuit element that provides resistance to the flow of charge
 - E) is a circuit element that measures the current in a circuit

2. Which combination of units can be used to express inductance?
 - A) $\text{T}\cdot\text{m}^2/\text{A}$
 - B) $\text{T}\cdot\text{m}/\text{A}$
 - C) $\text{T}^2\cdot\text{m}/\text{A}$
 - D) $\text{T}\cdot\text{m}/\text{A}^2$
 - E) $\text{T}^2\cdot\text{m}^2/\text{A}$

3. In an RL circuit, $\mathcal{E} = 9 \text{ V}$, $R = 30 \text{ }\Omega$, and $L = 6 \text{ mH}$. How much energy is stored in the inductor's magnetic field when the current reaches its maximum steady-state value?
 - A) Zero
 - B) $1.6 \times 10^{-4} \text{ J}$
 - C) $2.7 \times 10^{-4} \text{ J}$
 - D) $1.6 \times 10^{-3} \text{ J}$
 - E) $8.1 \times 10^{-3} \text{ J}$

4. When two circuits create magnetic flux through each other, what is the same for both circuits?
 - A) magnetic flux
 - B) current
 - C) mutual inductance
 - D) emf
 - E) capacitance

5. Which of the following does the inductance of an inductor depend on?
 - A) number of turns per length
 - B) length
 - C) radius
 - D) physical constants
 - E) all of the above

6. The Henry (H) is the SI unit for which of the following?
 - A) potential difference
 - B) magnetic field
 - C) electric field
 - D) current
 - E) inductance

7. At equilibrium, what is the voltage across an inductor?
 - A) zero
 - B) infinity
 - C) LI
 - D) $2LI$
 - E) LI^2

8. The time constant of an RL circuit is equal to
- A) LR
 - B) L/R
 - C) LR^2
 - D) L^2R
 - E) L^2/R
9. In an RL circuit as, $t \rightarrow \infty$, what does the current in the circuit approach?
- A) V/R
 - B) Zero
 - C) Infinity
 - D) LR
 - E) L/R
10. After an inductor in an RL circuit has been connected to a battery for a very long time, a switch is flipped causing the inductor to be connected to a resistor of resistance R . As $t \rightarrow \infty$, what does the current in the circuit approach?
- A) V/R
 - B) zero
 - C) infinity
 - D) LR
 - E) L/R
11. What is the equation for current growth in an inductor in an RL circuit?
- A) $I(t) = V/R$
 - B) $I(t) = (1 - e^{-(R/L)t})V/R$
 - C) $I(t) = (e^{-(R/L)t})V/R$
 - D) $I(t) = (1 + e^{-(R/L)t})V/R$
 - E) $I(t) = (e^{-(R/L)t} - 1)V/R$
12. What is the equation for current decay in an inductor in an RL circuit?
- A) $I(t) = V/R$
 - B) $I(t) = V/R(1 - e^{-(R/L)t})$
 - C) $I(t) = V/R(e^{-(R/L)t})$
 - D) $I(t) = V/R(1 + e^{-(R/L)t})$
 - E) $I(t) = V/R(e^{-(R/L)t} - 1)$
13. What is the equation for the magnitude of voltage across an inductor during current growth in an RL circuit?
- A) $V(t) = IR$
 - B) $V(t) = V_0(1 - e^{-(R/L)t})$
 - C) $V(t) = V_0e^{-(R/L)t}$
 - D) $V(t) = V_0(1 + e^{-(R/L)t})$
 - E) $V(t) = V_0(e^{-(R/L)t} - 1)$
14. What is the equation for the magnitude of voltage across an inductor during current decay in an RL circuit?
- A) $V(t) = IR$
 - B) $V(t) = V_0(1 - e^{-(R/L)t})$
 - C) $V(t) = V_0e^{-(R/L)t}$
 - D) $V(t) = V_0(1 + e^{-(R/L)t})$
 - E) $V(t) = V_0(e^{-(R/L)t} - 1)$
15. The voltage across an inductor is proportional to the
- A) current through the inductor
 - B) the resistance of the inductor
 - C) the charge on the inductor
 - D) the rate of change voltage across the inductor
 - E) the rate of change of current through the inductor

Answer Key
Lenz's LAW MC Questions [Mar 28, 2011]

1. C
 2. A
 3. C
 4. C
 5. E
 6. E
 7. A
 8. B
 9. A
 10. B
 11. B
 12. C
 13. C
 14. B
 15. E
-

Name _____

Class _____

Date _____

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____

8. _____

9. _____

10. _____

11. _____

12. _____

13. _____

14. _____

15. _____