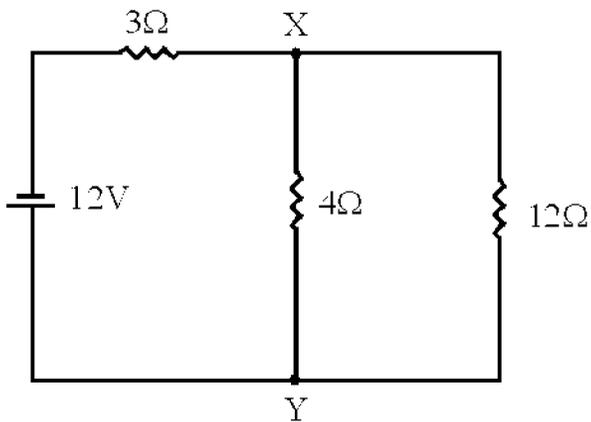


1. A circuit contains a 12 V power source, and a 3 Ω , 4 Ω , and 6 Ω , resistor. How should the resistors be arranged for the current through the battery to be 2 A?
- A) All resistors should be in series.
 - B) All resistors should be in parallel.
 - C) The 3 Ω and 4 Ω resistors should be in parallel, and the 6 Ω resistor in series.
 - D) The 3 Ω and 6 Ω resistors should be in parallel, and the 4 Ω resistor in series.
 - E) The 4 Ω and 6 Ω resistors should be in parallel, and the 3 Ω resistor in series.


2. Base your answer to the following question on the circuit diagram shown below.



What is the total resistance of the circuit?

- A) 1.5 Ω
- B) 6 Ω
- C) 8 Ω
- D) 14.4 Ω
- E) 19 Ω

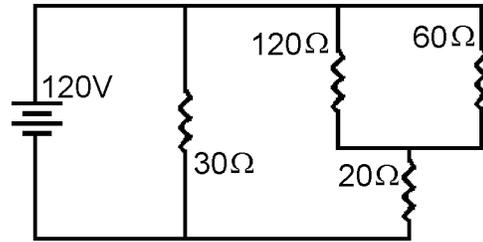3. Base your answer to the following question on the circuit shown below.




The equivalent resistance of this circuit most nearly

- A) 12 Ω
- B) 20 Ω
- C) 24 Ω
- D) 40 Ω
- E) 48 Ω

4. Base your answer to the following question on the diagram below which shows two different resistors, R_1 and R_2 , in two different connections to the same source of emf ϵ that has no internal resistance.

For each question(s) pick your answer from the following list.

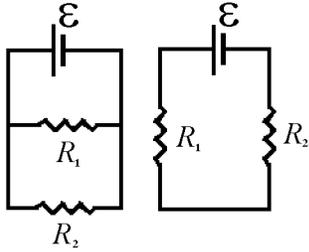
- I. It is greater for the parallel connection.
- II. It is greater for the series connection.
- III. It is the same for both connections.
- IV. It is different for each connection, but one must know the values of R_1 and R_2 , to know which is greater.
- V. It is different for each connection, but one must know the value of ϵ to know which is greater.



How does the equivalent resistance for these two cases compare?

- A) I
- B) II
- C) III
- D) IV
- E) V


5.

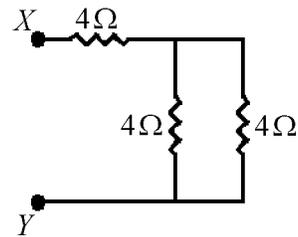

The total equivalent resistance between points X and Y in the circuit shown above is

- A) 6Ω
- B) 8Ω
- C) 10Ω
- D) 12Ω
- E) 14Ω


6.

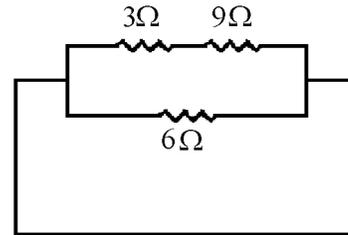

Determine the equivalent resistance of the above combination of resistors.

- A) 2Ω
- B) 4Ω
- C) 8 W
- D) 10 W
- E) 13 W


7.

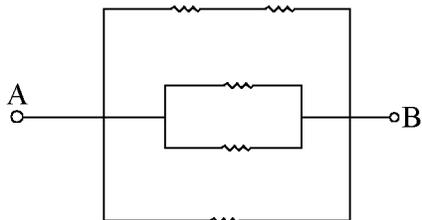

If all the above resistors have a resistance of R , determine the total equivalent resistance between points A and B .

- A) $\frac{2}{7}R$
- B) $\frac{2}{3}R$
- C) $\frac{3}{2}R$
- D) $\frac{5}{2}R$
- E) $\frac{7}{2}R$

8.

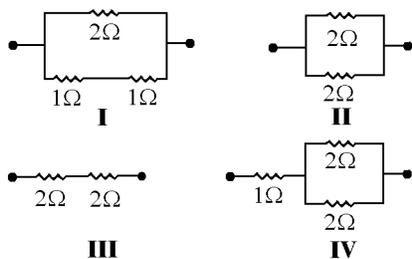

Which two arrangements of resistors shown above have the same resistance between the terminals?

- A) I and II
- B) I and III
- C) I and IV
- D) II and III
- E) III and IV

9. A circuit element that must be put in series and has a relatively low resistance is most likely

- A) an ammeter
- B) a voltmeter
- C) an ohmmeter
- D) either an ohmmeter or a voltmeter
- E) either a voltmeter or an ammeter

10. An ammeter does not appreciably affect the current of the circuit it is placed in because

- A) it is connected in parallel and has a high resistance
- B) it is connected in series and has a high resistance
- C) it is connected in parallel and has a low resistance
- D) it is connected in series and has a low resistance
- E) it is connected in either series or parallel and has no resistance

11. A voltmeter differs from an ammeter in that

- A) a voltmeter is connected in parallel and has much greater resistance
- B) a voltmeter is connected in series and has much greater resistance
- C) a voltmeter is connected in parallel and has much less resistance
- D) a voltmeter is connected in series and has much less resistance
- E) a voltmeter can be connected in parallel or in series

12. What combination of 4 Ω resistors can be used to create an equivalent resistance of 10Ω ?

- A) Two in parallel, in series with one
- B) Three in parallel
- C) Two in series, in parallel with one
- D) Two in parallel, in series with two
- E) Two in series, in parallel with two in series

13. A circuit is built using three resistors of resistance R .
Which of the following is a possible equivalent resistance
of the circuit?

A) $R/6$

B) $2R/3$

C) R

D) $2R$

E) $5R/2$

Answer Key
Drift Velocity MC Questions [Mar 28, 2011]

1. D
 2. B
 3. B
 4. B
 5. A
 6. B
 7. A
 8. A
 9. A
 10. D
 11. A
 12. D
 13. B
-

Name _____

Class _____

Date _____

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____

8. _____

9. _____

10. _____

11. _____

12. _____

13. _____