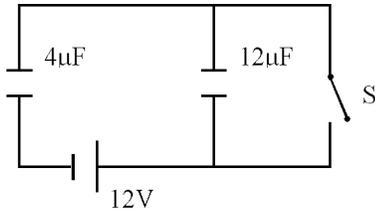


Base your answers to questions 1 through 4 on the following circuit diagram in which the battery has zero internal resistance.




- When switch S is open, what is the charge on the $4 \mu\text{F}$ capacitor?
 - $3 \mu\text{C}$
 - $4 \mu\text{C}$
 - $12 \mu\text{C}$
 - $36 \mu\text{C}$
 - $48 \mu\text{C}$
- When the switch S is open what is the total energy stored in the system?
 - 36 J
 - 216 J
 - 432 J
 - 1152 J
 - 2304 J
- When the switch S is closed, what is the energy stored in the $12 \mu\text{F}$ capacitor?
 - 0 J
 - 216 J
 - 432 J
 - 866 J
 - 1732 J

- When the switch S is open, what is the ratio of the energy stored in the $4 \mu\text{F}$ capacitor to the energy stored in the $12 \mu\text{F}$ capacitor?
 - $\frac{1}{9}$
 - $\frac{1}{3}$
 - 1
 - 3
 - 9

- Base your answer to the following question on the diagram below which shows two different capacitors, C_1 and C_2 , in two different connections to the same source of emf ϵ that has no internal resistance.

For each question pick your answer from the following list.

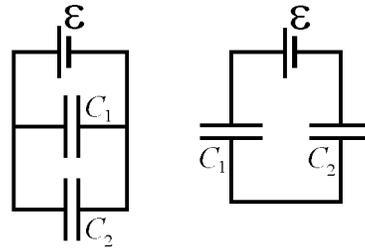- It is greater for the parallel connection.
- It is greater for the series connection.
- It is the same for both connections.
- It is different for each connection, but one must know the values of C_1 and C_2 , to know which is greater.
- It is different for each connection, but one must know the value of ϵ to know which is greater.



How does the total energy stored in the capacitors for these two cases compare?

- I
- II
- III
- IV
- V

6. A current of I flows through a resistor R for a time t . If all of the energy dissipated by the resistor is converted back into electrical energy by a perfectly efficient heat engine and a perfectly efficient generator and stored on a capacitor of capacitance C , how much charge is on the capacitor?

- A) $(CI^2Rt)^{1/2}$
- B) $(2CI^2Rt)^{1/2}$
- C) $2CI^2Rt$
- D) $(2I^2Rt/C)^{1/2}$
- E) $(2CI^2Rt)^2$

7. The energy stored in an isolated capacitor is

- A) the energy provided by the voltage source
 - B) the energy provided by the magnetic field
 - C) the energy provided by gravitational potential
 - D) the energy of the electric field between the plates
 - E) capacitors do not store energy
-

Answer Key
Energy in Resistor Circuits MC Questions [Mar 28, 2011]

1. D
 2. B
 3. A
 4. D
 5. D
 6. B
 7. D
-

Name _____

Class _____

Date _____

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____